

## Solving second order analogue filter

Second order polynomial:

$$P(s) = s^2 + 1.414s + 1$$

Coefficients:

$$a_1 = 1.414, a_0 = 1$$

Substitutions:

$$s = j2\pi\omega, \quad \omega c = 2\pi f c, \quad a_1 = \frac{1}{Q}, \quad \sqrt{a_0} = FSF$$

Hence,

$$Q = 0.707, \quad FSF = 1$$

For filter with gain K=1, equations from Texas Instruments:

$$FSF \times f_c = \frac{1}{2\pi RC\sqrt{mn}}, \quad Q = \frac{\sqrt{mn}}{m+1} \quad \text{where} \quad R_1 = mR, R_2 = R, C_1 = C, C_2 = nC$$

Solving for ratio of m and n

$$0.707 = \frac{\sqrt{mn}}{m+1}$$

$$0.707^2 = \frac{mn}{m^2 + 2m + 1}$$

$$0.707^2 m^2 + (2 \times 0.707^2 - n)m + 0.707^2 = 0$$

$$m = \frac{n - 2 \times 0.707^2 + \sqrt{(2 \times 0.707^2 - n)^2 - 4 \times 0.707^4}}{2 \times 0.707^2}$$

The above gives us a graph for n to m ratio. Here we are free to pick any convenient ratio for the filter.

$$\text{Choose} \quad n = 2, m = 1$$

$$\text{Desired} \quad f_c = 25\text{Hz}$$

Substituting in the equations from Texas Instruments to obtain C and R near standard values:

$$25 = \frac{1}{\sqrt{2} \times 2\pi RC}$$

$$\text{Choose} \quad C = 2.2 \mu F \text{ (standard value)}$$

$$R = \frac{1}{\sqrt{2} \times 25 \times 2\pi \times 2.2 \times 10^{-6}} = 2046 \approx 2K \text{ (standard value as well)}$$

$$\text{Results: } R_1 = 2K, R_2 = 2K, C_1 = 2.2\mu F, C_2 = 4.7\mu F$$

Check the actual cutoff frequency  $f_c$

$$f_c = \frac{1}{2\pi \times 2 \times 10^3 \times \sqrt{2.2 \times 4.7 \times 10^{-6}}} = 24.7 \text{ Hz} \quad \text{near expected } f_c$$

### Appendix:

Graph for n and m

